

Total No. of Questions : 8]

[Total No. of Printed Pages : 4]

Roll No .....

**EC-3003 (CBGS)****B.E. III Semester**

Examination, December 2017

**Choice Based Grading System (CBGS)****Network Analysis****Time : Three Hours****Maximum Marks : 70****Note:** i) Attempt any five questions.

ii) All questions carry equal marks.

1. a) Calculate the voltage (V) in the circuit of Figure 1.

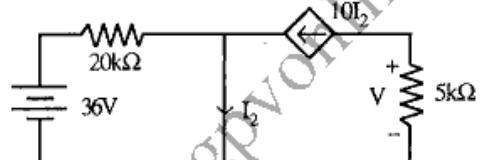


Figure 1

- b) Determine I in the circuit shown in Figure 2.

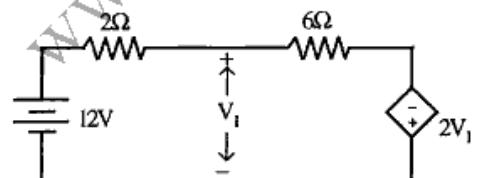


Figure 2

- c) Write the KCL equations for the circuit shown in Figure 3.

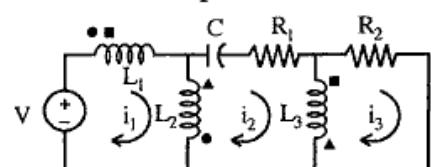


Figure 3

2. a) For the network shown in Figure 4, draw network graph. Obtain the basic cutsets and write basic cutset matrix.

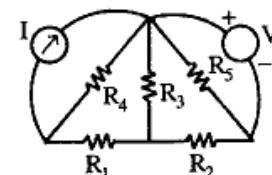


Figure 4

- b) For the network shown in Figure 5. Obtain the incidence matrix, the node admittance matrix and the matrix node equation.

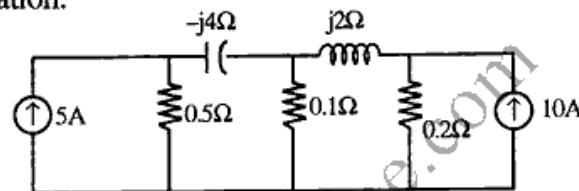


Figure 5

3. a) Find the Norton equivalent of the network shown in Figure 6.

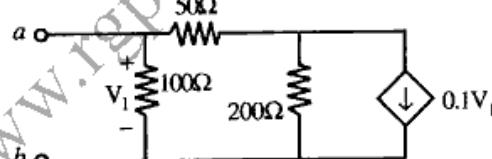


Figure 6

- b) Determine the value of  $R_L$  to be connected across AB in Figure 7, for maximum power transfer. Also calculate the maximum power absorbed by  $R_L$ .

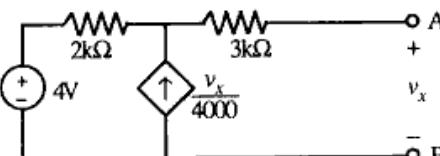


Figure 7

Contd....

[3]

4. a) State and prove reciprocity, and compensation theorems.  
 b) State and prove Tellegen's theorem.
5. a) Find the current  $i(t)$  for the network shown in Figure 8 if the voltage source  $v(t) = 2e^{-0.5t} u(t)$  and  $v_c(0^+) = 0$

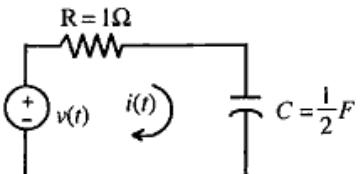


Figure 8

- b) At  $t = 0$ , switch S is closed in the circuit of figure 9, find  $v_c(t)$  and  $i_c(t)$ . All initial conditions are zero

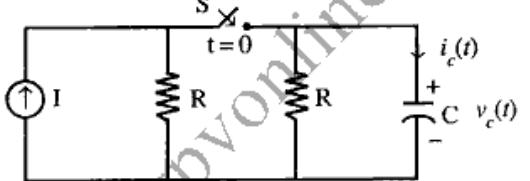


Figure 9

6. Calculate the current in  $6\Omega$  resistor of the circuit of Figure 10 by

- i) Thevenin's theorem  
 ii) Superposition theorem

Use Laplace transform method:

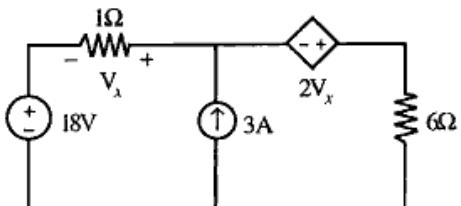


Figure 10

[4]

7. a) Determine the Z-parameters for the network shown in figure 11.

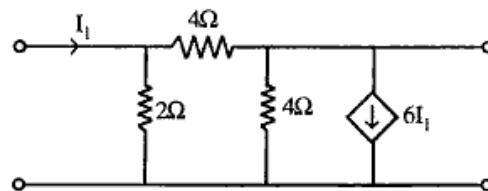


Figure 11

- b) Obtain the Z-parameters of the network shown in figure 12.

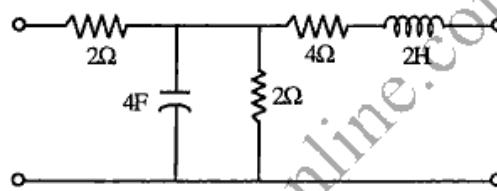


Figure 12

8. Write short notes on any two of the following:

- a) Parallel resonance  
 b) Maximum power transfer theorem  
 c) Hybrid parameters

\*\*\*\*\*

182