

Roll No.

EC-403(N)**B. E. (Fourth Semester) EXAMINATION, Dec., 2010****(New Scheme)****(Electronics & Communication Engg. Branch)****DIGITAL ELECTRONICS****[EC-403(N)]***Time : Three Hours**Maximum Marks : 100**Minimum Pass Marks : 35*

Note : Attempt all questions. All questions have choice. All questions carry equal marks.

1. Convert the following terms : 20

- (i) $(153.6875)_{10} = ()_8$
- (ii) $(26153.7406)_8 = ()_{16}$
- (iii) $(630.4)_8 = ()_{10}$
- (iv) $(60236002)_8$ divide by $(256)_8$
- (v) $(7643)_8 = ()_2$
- (vi) $(001111001010101)_2 = ()_{16}$

Or

Explain the following methods : 10, 10

- (i) Karnaugh's map method
- (ii) Quine and McCluskey's method

2. (a) Describe full adder and full subtractor with diagram and table. 10
- (b) Explain multiplexer and demultiplexer. 10

Or

- (a) Discuss design and analysis of combinational circuit. 10
- (b) Minimize the following function using Karnaugh map and realize the minimized function using NOR gates : 10

$$F(A, B, C, D) = B\bar{C} + \bar{A}B + BCD + \bar{A}\bar{B}D + A\bar{B}\bar{C}D$$

3. (a) What is multivibrator ? Explain monostable and bistable multivibrator. 10
- (b) Define flip-flop. Give their types and explain JK-flip-flop in details. 10

Or

Explain the following terms : 20

- (i) D-flip-flop
- (ii) Synchronous and asynchronous counters
- (iii) Johnson and ring counter
4. What is computer memory ? Give classification of memory system. Discuss EEPROM, PAL and PLAs. 20

Or

Explain the construction and organization of the following memories : 20

- (i) SRAM
- (ii) DRAM
- (iii) ROM
- (iv) PROM

[3]

5. (a) Compare the following logic families :
RTL, DTL, TTL and ECL. 10
- (b) Describe PMOS, NMOS and CMOS logic. 10

Or

Write short notes on the following : 20

- (a) Universal gates
- (b) Clocked R-S flip-flop
- (c) Binary ripple counter