

Total No. of Questions : 10 ] [ Total No. of Printed Pages : 3

Roll No. ....

## EC-403

B. E. (Fourth Semester) EXAMINATION, June, 2012

(Grading/Non-Grading)

(Electronics & Communication Engg. Branch)

DIGITAL ELECTRONICS

(EC-403)

Time : Three Hours

Maximum Marks :  $\begin{cases} GS : 70 \\ NGS : 100 \end{cases}$

Note : Attempt *one* question from each Unit. All questions carry equal marks.

### Unit-I

1. (a) Convert the following in the radix shown :

(i)  $(444.456)_{10} = ( )_8$

(ii)  $(101111.1101)_2 = ( )_{10}$

(b) Express the function  $Y = A + \bar{B}C$  in (i) canonical SOP and (ii) canonical POS form.

(c) Simplify the expression :

$$Y = \sum_m (7, 9, 10, 11, 12, 13, 14, 15)$$

using the K-map method.

Or

2. (a) Add the following BCD numbers :

(i) 1001 and 0100

(ii) 00011001 and 00010100

P. T. O.

(b) Realise :

(i)  $Y = A + B\bar{C}\bar{D}$  using NAND gates

(ii)  $Y = (A + C)(A + \bar{D})(A + B + \bar{C})$  using NOR gates

**Unit - II**

3. (a) Discuss the design of BCD adder.

(b) Discuss the use of MUX for generating the function :

$$Y = \bar{A}\bar{B}\bar{C}D + BCD + A\bar{B}\bar{C} + ABCD$$

*Or*

4. (a) With the help of circuit diagram explain the working of 4 bit parallel adder.

(b) Design a full subtractor using logic gates.

**Unit - III**

5. (a) Design an Astable multivibrator using 555 timer and explain its working.

(b) Design a MOD-8 counter using JK flip-flop.

*Or*

6. (a) Explain the working of master slave JK flip-flop.

(b) Design a MOD-7 counter using T flip-flop.

**Unit - IV**

7. Discuss the following memories :

(a) SRAM

(b) PAL

(c) EPROM

*Or*

8. Discuss the following semiconductor memories :

(a) DRAM

(b) EEPROM

(c) PLA

[ 3 ]

Unit-V

9. (a) Explain the operation of emitter coupled logic.  
(b) Discuss the operation of n-channel MOS logic circuits.

Or

10. (a) Construct a circuit with TTL as a driver and CMOS as a load and explain.  
(b) Explain with the aid of a circuit diagram the operation of a TTL-3 input NAND gate.

