

Roll No .....

**EC - 403****B.E. IV Semester Examination, June 2014****Digital Electronics***Time : Three Hours***Maximum Marks : 70**

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.  
 ii) All parts of each question are to be attempted at one place.  
 iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.  
 iv) Except numericals, Derivation, Design and Drawing etc.

**Unit - I**

1. a) Convert the following as directed. 2
  - i)  $[10110]_2$  to  $[\quad]_{\text{gray}}$
  - ii)  $[11010101.10011]_2$  to  $[\quad]_8$
- b) Subtract  $(1010)_2$  from  $(1000)_2$  using 2's complement method. Subtract by direct method also and compare the result. 2
- c) Express the function  $Y = A + \bar{B}C$  in (i) canonical SOP and (ii) canonical POS form. 3
- d) Simplify the expression  $Y = \sum_m (3, 4, 5, 7, 9, 13, 14, 15)$  using K-map method. 7

**OR**

Find the minimal sum of product, for the Boolean expression  $f = \sum (1, 2, 3, 7, 8, 9, 10, 11, 14, 15)$  using the Quine-McCluskey method. 7

**Unit - II**

2. a) Realise  $Y = (A + C)(A + \bar{D})(A + B + \bar{C})$  using NOR gates. 2
- b) Design a half adder. 2
- c) Design a full subtractor using logic gates. 3
- d) Design BCD adder using full adders. 7

**OR**

Implement the function  $F(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15)$  using multiplexer. 7

**Unit - III**

3. a) Explain briefly the working of R-S flip flop. 2
- b) Give the applications of 555 timer chip. 2
- c) Discuss the working of J-K flip flop with the help of circuit diagram, state and excitation table. Also explain the race around condition. 3
- d) With the help of circuit diagram and timing diagram explain the working of Monostable multivibrator designed using transistors. 7

[2]

OR

Design a Modulo-7 counter using J-K flip flop.

7

**Unit - IV**

- |       |  |   |
|-------|--|---|
| 4. a) | Give a broad classification of semiconductor memories.               | 2 |
| b)    | Give the construction of RAM.  | 2 |
| c)    | On the basis of organisation and construction compare SRAM and DRAM. | 3 |
| d)    | Discuss the working and construction of RAMBUS ROM and PAL.          | 7 |

OR

Discuss the working and construction of PROM and PLA's.

7

**Unit - V**

- |       |  |   |
|-------|--|---|
| 5. a) | Give the characteristics of RTL family.  | 2 |
| b)    | Give two advantages and disadvantages of totem pole output arrangements.           | 2 |
| c)    | Explain briefly about ECL logic family.  | 3 |
| d)    | Explain briefly the characteristics of MOS logics and write a note on CMOS logics. | 7 |

OR

Compare the characteristics of different logic families.

7

\*\*\*\*\*