

Roll No

EC - 505

B.E. V Semester

Examination, December 2012

Communication Network And Transmission Lines

Time : Three Hours

Maximum Marks : 70/100

Note : 1. Attempt one question from each unit.

2. All questions carry equal marks.

Unit - I

1. a) Determine the image impedance, iterative impedance and characteristic impedance of symmetrical two port network.
- b) Discuss the design of symmetrical attenuators. Also discuss their working principle.

OR

2. a) Differentiate between image transfer coefficient and iterative transfer coefficient.
- b) Discuss the different matching techniques.

Unit - II

3. Discuss the designing of following filters:
 - a) m-derived filters.
 - b) Chebyshev approximation.

OR

4. Discuss the designing of the following filters:
 - a) Composite filter.
 - b) Butterworth approximation.

Unit - III

5.
 - a) Explain briefly about Foster and cancer network.
 - b) What is Bott Duffin method? Explain.

OR

6.
 - a) What do you understand by minimum positive real function?
 - b) Explain Brune's method.

Unit - IV

7.
 - a) Explain briefly about attenuation and phase equalizers.
 - b) Discuss briefly about the T and Z equivalents of a line.

OR

8.
 - a) Explain briefly about open circuit and short circuit line.
 - b) Discuss about the different losses in transmission lines.

Unit - V

9. Write short notes on the following:
 - a) SWR
 - b) Double stub matching

OR

10. Write short notes on the following:
 - a) Quarter wave line.
 - b) Microstrip lines.
