

Total No. of Questions : 8]

[Total No. of Printed Pages : 2

Roll No .....

**EE-504 (GS)****B.E. V Semester**

Examination, December 2017

**Grading System (GS)****Digital Electronics and Logic Design****Time : Three Hours****Maximum Marks : 70**

- Note:** i) Attempt any five questions.  
ii) Each question having equal marks.

- What are meant by the 1's and 2's complements of a binary numbers. Determine the number of bits required to represent in floating point notation the exponent for decimal numbers in the range of  $10^{\pm 86}$ .
  - How are binary digits used to express the integer and fraction part of a number? Subtract  $(1010)_2$  from  $(1111)_2$  using the 2's complement method and subtract by direct method also and compare.
- What do you mean by weighted binary codes. Explain BCD or 8421 Code with suitable example?
  - What is a Hamming code and how is it used? A 7-bit Hamming code is received as 0101101. What is its correct code?
- Verify that the following operations are commutative but not associative
    - NAND
    - NOR
 Also prove the following Boolean Expression
 
$$(A + B)(\overline{A}\overline{C} + C)(\overline{B} + AC) = \overline{A}B$$
  - Draw the basic BiCMOS inverter and explain its operation.

EE-504 (GS)

145

PTO

[2]

- Explain "4-bit Binary-to-gray code converter".
  - Obtain the minimum sum of products expression for the following function and implement the same using universal gates.  

$$f(A, B, C, D) = \sum(0, 2, 3, 5, 7, 8, 13) + \sum d(1, 6, 12)$$
- Draw the logic diagram of master-slave D flip-flop using NAND gates.
  - Realize J-K flip-flop using T flip-flop.
- What is a ripple counter? Draw the gates necessary to decode all the stages of a MOD-16 counter using active-LOW outputs.
- Explain the working of serial in parallel out shift register with logic diagram and waveform.
  - Design a sequence generator to generate the sequence 1001.
- Write short note (any two):
  - EPROM (Erasable Programmable ROM)
  - PSRAM (Pseudo Static RAM)
  - Dual-Slop Analog and Digital Converter

\*\*\*\*\*

EE-504 (GS)

HTTP://WWW.RGPVONLINE.COM