

Roll No.

EX-403(N)

RGPVONLINE.COM

B. E. (Fourth Semester) EXAMINATION, June, 2011

(Electrical & Electronics Engg. Branch)

DIGITAL ELECTRONICS LOGIC DESIGN-I

[EX-403(N)]

Time : Three Hours

Maximum Marks : 100

Note : Attempt any five questions. All questions carry equal marks.

1. (a) Perform the following operations by 9's and 10's complement method.: 10
 - (i) $110 - 87$
 - (ii) $464.8 - 279.7$
- (b) Convert the following decimal numbers to octal : 10
 - (i) 185
 - (ii) 64.25
2. (a) Add the following in BCD code : 10
 - (i) $185 + 396$
 - (ii) $104.7 + 185.65$
- (b) Determine the single error correcting code for the BCD number 10110 for odd parity. 10
3. (a) Sketch the circuit for a simple bipolar transistor inverter. Sketch phase relationship between the input and output pulse wave forms. 10

P. T. O.

[2]

<http://www.rgpvonline.com>

- (b) Draw the logic diagram and construct the truth table for the following : 10
 - (i) $AB(\overline{A+B}) + \overline{EF}$
 - (ii) $\overline{AB} + C\overline{D} + ABC$
4. (a) Reduce the following Boolean expression : 10

$$(X + Y + Z)(\overline{X} + \overline{Y} + \overline{Z})X$$
- (b) Show that both NAND gate and NOR gate are universal gate. 10
5. (a) Obtain the minimal SOP expression for :

$$\Sigma m(2, 3, 5, 7, 9, 11, 12, 13, 14, 15)$$
 and implement in NAND logic. 10
- (b) What do you mean by Min terms and Max terms of Boolean expression ? 10
6. (a) Design the 4 bit magnitude comparator with the help of logic diagram. RGPVONLINE.COM 10
- (b) Draw truth table and logic diagram for BCD to Decimal Decoder. 10
7. (a) What do you mean by Flip-Flop.? How does JK flip-flop differ from S-R flip-flop ? 10
- (b) Implement a 3 bit ripple counter using flip-flop. 10
8. (a) What is ROM ? Explain different types of ROM and its uses. 10
- (b) With the help of neat diagram explain the working of successive approximation ADC. 10

EX-403(N)

6,250