

Roll No _____

EX - 403

B.E. IV Semester

Examination, June 2014

Digital Electronics Logic Design - I

Time : Three Hours

Maximum Marks : 70

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
ii) All parts of each question are to be attempted at one place.
iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.
iv) Except numericals, Derivation, Design and Drawing etc.

Unit - I **RGPVONLINE.COM**

1. a) Determine the decimal numbers represented by the following binary numbers.
i) 1100.1011 ii) 1001.0101 2
 - b) Convert the following octal number into equivalent decimal numbers.
i) 237 ii) 0.75 2
 - c) Explain basic theorems of Boolean Algebra. 3
 - d) Given the logic equation
$$f = ABC + \bar{B}\bar{C}D + \bar{A}BC$$

i) Make a truth table ii) Simplify using k-map
iii) Realized using NAND gates. 7
- OR
- i) Why ASCII code is a 7 bit code.
 - ii) Explain different logic gates with their graphical symbol, algebraic function and truth table. 7

Unit - II

2. a) What is meant by a combinational circuit? 2

- | | |
|---|---|
| b) Draw the circuit diagram for half adder? | 2 |
| c) Explain working of full subtractor with block diagram. | 3 |
| d) Draw the block diagram of BCD adder and explain its working. | 7 |

OR

What is multiplexers? Design 4 to 1 line multiplexer with logic diagram and function table.

Unit - III

3. a) What is a flip-flop? How many flip-flops are required for storing n bit of information. 2
- b) What is meant by race around condition in flip-flop. 2
- c) What are the various methods used for triggering of flip-flops. 3
- d) Draw the circuit diagram of J-K flip flop and explain its working. What are limitation of JK flip flop. 7

OR

Explain design procedure for sequential circuit with suitable example. 7

Unit - IV

4. a) What is a shift register? Mention some application of shift register. 2
- b) Differentiate between synchronous and asynchronous counters. 2
- c) Draw the state diagram of a 3 bit binary counter. 3
- d) Explain the working of Johnson counter with suitable block diagram. 7

OR

Explain the operation of a 5 stage twisted ring counter.

Unit - V

5. a) What are the different types of read only memories. 2
- b) Explain PLA in short. 2
- c) What are the advantages of dynamic RAM over static RAM. 3
- d) List different methods of A/D conversion? Also explain successive approximation method in detail. 7

OR

Explain the following (any two)

- i) D/A converters, ii) PAL iii) RAM