

Total No. of Questions : 8]

[Total No. of Printed Pages : 3

Roll No .....

## EC-3003-CBGS

### B.E. III Semester

Examination, December 2020

### Choice Based Grading System (CBGS)


### Network Analysis

Time : Three Hours


Maximum Marks : 70

- Note:** i) Attempt any five questions.  
ii) All questions carry equal marks.

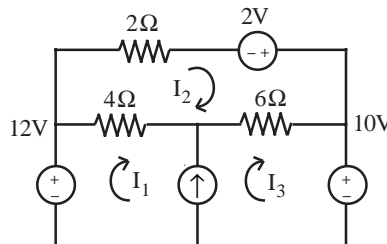1. a) State KCL and KVL and determine the mesh current  $I_1$ ,  $I_2$  and  $I_3$ .




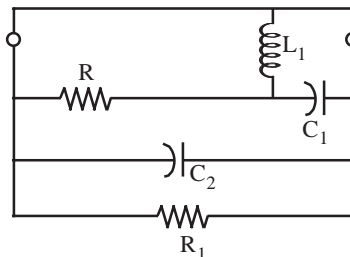- b) Define graph of the network and draw the graph for the given circuit.




2. a) Determine the Thevenin's equivalent circuit across 'AB' for given circuit.

[2]

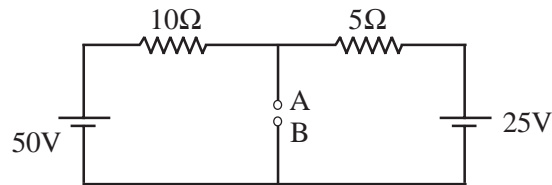


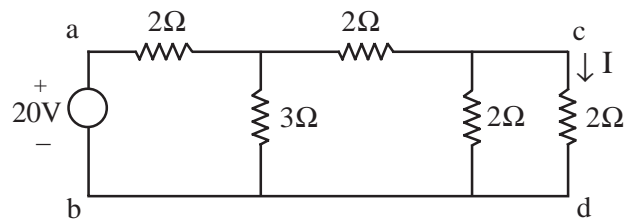- b) Verify the reciprocity theorem for the network shown in figure.



3. a) Explain the Transient analysis of series RL circuit.
- b) A series RC circuit consists of resistor of  $10\Omega$  and capacitor of  $0.1F$  as shown in figure. A constant voltage of  $20V$  is applied to the circuit at  $t = 0$ . obtain the current equation. Determine the voltages across the resistor and the capacitor.
4. What are the uses of knowing initial conditions in a circuit?  
Explain the initial conditions in
  - i) Resistor
  - ii) Inductor
  - iii) Capacitor

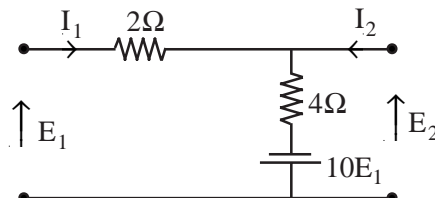5. a) The  $z$  parameters  $z_{11}$  and  $z_{21}$  for the 2-port networks in figure are:



EC-3003-CBGS

Contd....

[3]

- b) Derive hybrid parameters in terms of z-parameters.
6. Discuss the following in brief:
- a) Network graph, tree, branch, link and incidence matrix
  - b) Node analysis and Mesh analysis
7. Write short notes (any two)
- a) Millman's theorem and reciprocity theorem
  - b) Various kinds of sources
  - c) Dual networks
  - d) Initial and final value theorems
  - e) Y-parameters in terms of h-parameters
8. Write short notes on any two of the following:
- a) Parallel resonance
  - b) Maximum power transfer theorem
  - c) Hybrid parameters

\*\*\*\*\*