

Total No. of Questions : 10] [Total No. of Printed Pages : 3

Roll No.

EC-505

B. E. (Fifth Semester) EXAMINATION, Dec., 2011
(Electronics & Communication Engg. Branch)

CMOS VLSI DESIGN

(EC-505)

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt any *one* question from each Unit. All Units are compulsory to attempt. All questions carry equal marks.

Unit-I

1. (a) Explain the CMOS Inverter D. C. characteristic. How CMOS Inverter can be used as amplifier ? 10
- (b) Determine the type and the amount of Channel Ion Implantations which are necessary to achieve a threshold voltage of $V_{T0} = -2\text{ V}$ for P-Channel mosfet with the following parameters : 10
 - (i) Substrate doping density $N_A = 10^{15}/\text{cm}^3$
 - (ii) Polysilicon gate doping density $N_D = 10^{20}/\text{cm}^3$
 - (iii) $T_{OX} = 650\text{ \AA}$
 - (iv) $N_{OX} = 4 \times 10^{10}/\text{cm}^2$

Also calculate threshold voltage V_{T0} for $V_{SB} = 0$.

P. T. O.

Or

2. (a) Write short notes on the following : 12
- (i) Stick diagrams
 - (ii) Channel length modulation
 - (iii) Pass transistor
 - (iv) Tunneling
- (b) Explain briefly the MOS capacitance model. 8

Unit – II

3. (a) Explain the following terms in reference of VLSI technology : 20
- (i) Wafer formation
 - (ii) Photolithography
 - (iii) Oxidation
 - (iv) Isolation
 - (v) Well and Channel formation

Or

4. (a) What are VLSI interconnects ? How interconnects are developed during IC fabrication ? 10
- (b) What are design rules ? Explain MOSIS Design rule. 10

Unit – III

5. (a) Explain Elmore's delay model for estimation of parasitic delay in CMOS circuit. 10
- (b) Explain the following terms with respect to CMOS chip design : 10
- (i) Capacitance
 - (ii) Process variation
 - (iii) Temperature
 - (iv) Reliability

[3]

Or

6. (a) What is power dissipation in CMOS ? Explain static power dissipation and its cause. Explain different methods to reduce it. 12
(b) Explain the following terms : 8
(i) Transmission sizing
(ii) Interconnect scaling

Unit – IV

7. (a) What are CMOS Op-Amp. and RF circuits ? Explain them briefly. 10
(b) What are differential pairs ? Explain them in brief with mathematical expression ? 10

Or

8. (a) What are current mirrors ? Derive expression for it. 10
(b) Explain the following : 10
(i) MOS Small Signal Model
(ii) CMOS designed Analog to Digital Converter

Unit – V

9. Explain the following terms : 20
(i) Cell Hierarchies
(ii) Cell Shapes
(iii) Ratioed circuit
(iv) Cascode Voltage Switch logic

Or

10. What is BICMOS logic ? Derive the expression for switching delay in BICMOS logic circuit ? Explain different applications of BICMOS. 20