

rgpvonline.com

Roll No

EC - 605(NGS)

B.E. VI Semester

Examination, June 2013

Communication Network & Transmission Lines

(Non-Grading Scheme)

Time : Three Hours

Maximum Marks : 100

Minimum pass Marks: 35

Note: Attempt any five questions. All questions carry equal marks.

1. Discuss the following parameter of symmetrical two port networks.
 - a) Image impedance rgpvonline.com
 - b) Iterative impedance
 - c) Characteristic impedance
 - d) Propagation coefficient

2.
 - a) Discuss about the matching techniques in communication networks.
 - b) Explain the working of a symmetrical alternators.

3.
 - a) Discuss the designing of band pass filter.
 - b) Explain the working of m-derived filter.

rgpvonline.com [2]

4.
 - a) Discuss briefly about the designing of composite filter.
 - b) Explain briefly about Butter worth approximation.

5.
 - a) Discuss briefly about foster carer networks.
 - b) Explain briefly about Brune's method.

6.
 - a) Discuss the principle working of phase equalizer.
 - b) How to locate line fault. rgpvonline.com

7.
 - a) Characterize the voltage and current on a dissipation less line.
 - b) How to measure power and impedance of a line?

8. Write short notes on any two of the following :
 - a) Minimum positive real function
 - b) T and π equivalents of line
 - c) Stub matching

rgpvonline.com