

6. Determine the Fourier series of the waveform shown in figure 9.

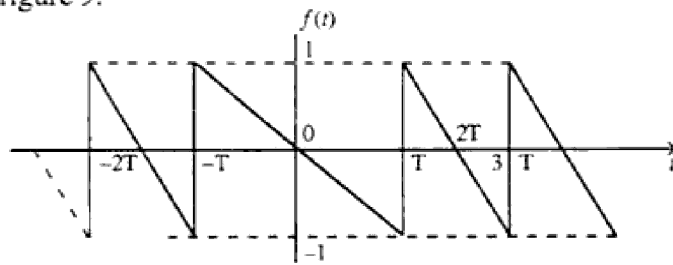


Figure 9

7. a) Determine the Z-parameters of the network shown in figure 10.

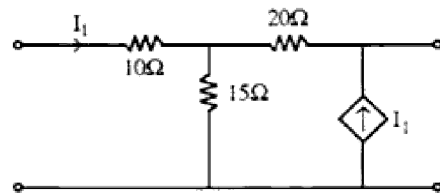


Figure 10

- b) Obtain the Z-parameters of the network shown in figure 11.

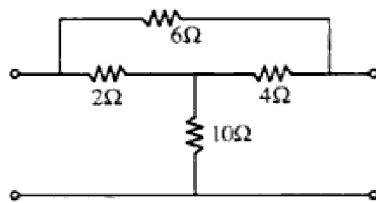


Figure 11

8. Write short notes on any two of the following :
- Series and Parallel resonance
  - Maximum power transfer theorem
  - Hybrid parameters

\*\*\*\*\*

Roll No .....

**EE/EI/IC/EX-305**

**B.E. III Semester**

**Examination, December 2016**

**Network Analysis**

**Time : Three Hours**

**Maximum Marks : 70**

- Note:** i) Attempt any five questions.  
ii) All questions carry equal marks.

1. a) In the circuit of figure 1 the switch S is moved from position 1 to 2 at  $t = 0$ , having been in position 1 for a long time before  $t = 0$ . Capacitor  $C_2$  is uncharged at  $t = 0$ .
- Find the particular solution for  $i(t)$  for  $t > 0$ .
  - Find the particular solution for  $V_2(t)$  for  $t > 0$ .

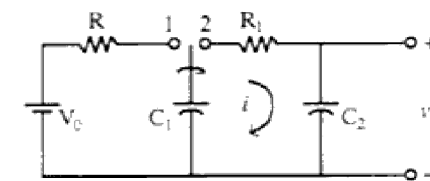


Figure 1

- b) In the circuit of figure 2, the switch S is open and the circuit reaches a steady state. At  $t = 0$  the switch S is closed. Find the current in the inductor for  $t > 0$ .

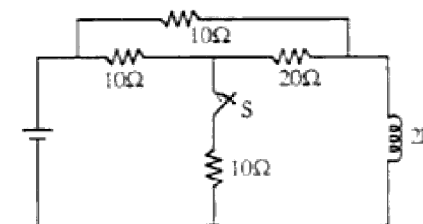


Figure 2

[2]

2. a) In the circuit of figure 3 the switch is opened at  $t = 0$ . Find the following quantities at  $t = 0^+$ .

- i)  $v_1$  ii)  $v_2$   
iii)  $\frac{dv_1}{dt}$  iv)  $\frac{dv_2}{dt}$

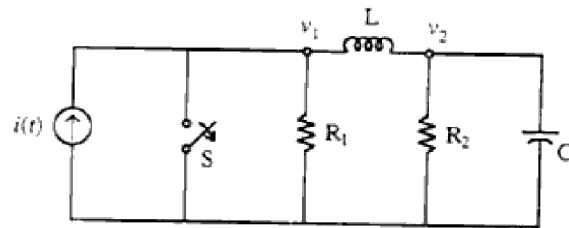


Figure 3

- b) In the circuit shown in figure 4, the capacitor  $C_1$  is charged to voltage  $V_0$  and the switch  $S$  is closed at  $t = 0$ . When  $R_1 = 2\text{M}\Omega$ ,  $V_0 = 1000\text{V}$ ,  $R_2 = 1\text{M}\Omega$ ,  $C_1 = 10\text{ }\mu\text{F}$  and  $C_2 = 20\text{ }\mu\text{F}$ , solve for  $i_2$ ,  $\frac{di_2}{dt}$  and  $\frac{d^2i_2}{dt^2}$  at  $t = 0^+$ .

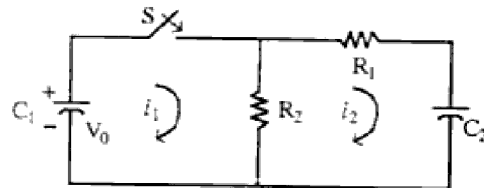


Figure 4

3. a) Find the Norton equivalent circuit across terminal AB of the circuit shown in figure 5.

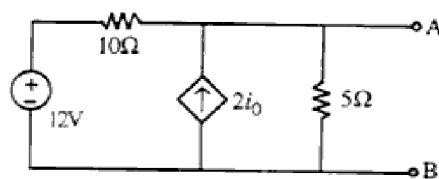


Figure 5

[3]

- b) Find the value of  $Z_L$  to have maximum power transfer from  $10\angle 0^\circ\text{V}$  voltage sources. Also determine the amount of maximum power in figure 6.

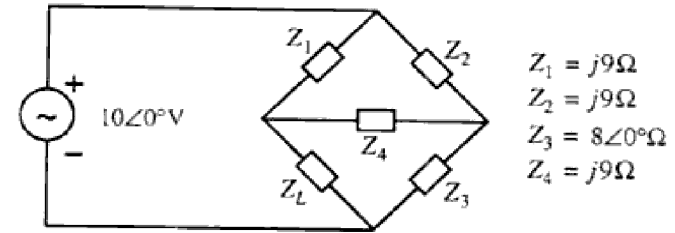


Figure 6

4. a) State and prove superposition and reciprocity theorem.  
b) State and prove Millman's theorem and Tellegen's theorem.
5. a) In the circuit of figure 7, the switch  $S$  is closed at  $t = 0$  with the capacitor initially unenergised for the numerical values given find  $i(t)$

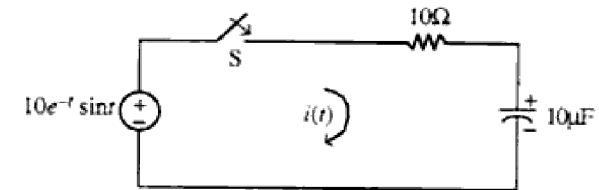


Figure 7

- b) Find the Laplace transform of the waveforms shown in figure 8.

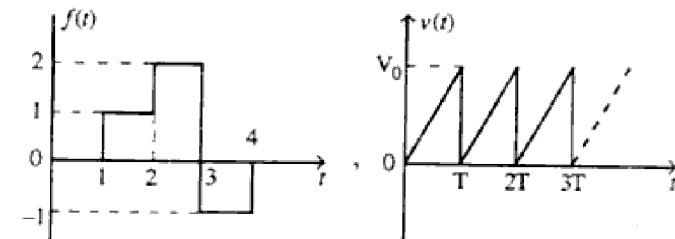


Figure 8 (a, b)