

Roll No.

EX-403

**B. E. (Fourth Semester)
EXAMINATION, June, 2012**

(Grading/Non-Grading)

(Electrical & Electronics Engg. Branch)

DIGITAL ELECTRONICS AND LOGIC DESIGN – I

(EX-403)

Time : Three Hours

Maximum Marks : $\begin{cases} GS : 70 \\ NGS : 100 \end{cases}$

Note : Attempt one question from each Unit. All questions carry equal marks.

Unit – I

1. (a) Convert the following numbers to the numbers of the base shown below :
 - (i) $(53.625)_{10} = ()_2$
 - (ii) $(444.456)_{10} = ()_8$
 - (iii) $(A3B)_{16} = ()_8$
 - (iv) $(1010111)_2 = ()_{10}$
- (b) Using the K-map method, simplify the following Boolean function and obtain :
 - (i) Minimal SOP
 - (ii) Minimal POS expression :


$$Y = \sum_m (0, 2, 3, 6, 7) + \sum_d (8, 10, 11, 15)$$

P. T. O.

[2]

Or

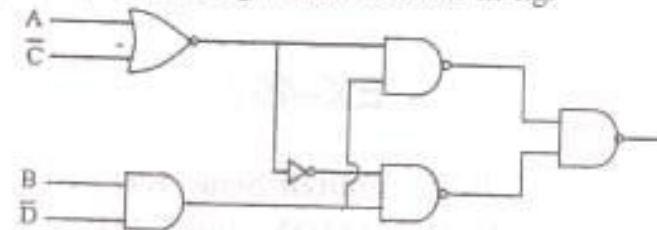2. (a) Simplify the logic circuit shown in fig.



- (b) Simplify the expression :

$$\overline{A \overline{B} + ABC + A(B + A \overline{B})}$$

Unit – II

3. (a) Design a full subtractor using logic gates.
- (b) Implement the Boolean expression :

$$Y = \Sigma (0, 2, 4, 5, 7, 12)$$
 using multiplexer.

Or

4. (a) Design and explain look ahead carry generator.
- (b) Explain the working of serial adder and subtractor.

Unit – III

5. (a) With the help of block diagram and waveform explain the working of clocked J-K flip-flop.
- (b) What is Race around condition and how it could be eliminated ?

Or

6. (a) What is meant by edge triggering ? Discuss the working of the edge triggering circuit.
- (b) Explain the working of S-R flip-flop. Also draw its state diagram and write its characteristic equation.

Unit – IV

7. (a) Design a MOD-7 counter using T flip-flop.
- (b) Explain the working of shift left-shift right registers.

Or

8. (a) Explain the working of BCD counter.
- (b) Compare the performance of synchronous and asynchronous counter.

Unit – V

9. (a) Explain the working of static RAM cell using MOS transistor.
- (b) Explain the working of successive approximation type analog to digital converter.

Or

10. (a) Write a short note on PAL.
- (b) Explain the working of Binary weighted digital to analog converters.

RGPVONLINE.COM