

Total No. of Questions :8]

[Total No. of Printed Pages :2

Roll No .....

**EX-504**

**B.E. V Semester**

Examination, December 2016

**Power Electronics Devices and Circuits**

**Time : Three Hours**

**Maximum Marks : 70**

Note: i) Answer any five questions.

ii) All questions carry equal marks.

1. a) Describe the different modes of operation of a thyristor with the help of its static V-I characteristics. 7  
b) Define latching and holding currents as applicable to an SCR. Show these currents on its static V-I characteristics. 7
2. a) Explain the different applications of: 7  
i) Power MOSFET  
ii) IGBT  
iii) GTO  
iv) SCR  
b) Explain the need of commutation in thyristor circuits. 7  
Name the different methods of commutation schemes. Explain any one method.
3. a) Explain with circuit diagram of a single phase full converter bridge with RLE load. Draw voltage and current waveforms for continuous load currents? for  $\alpha > 90^\circ$ . 7  
b) Discuss the effect of source inductance on the performance of a single phase full converter indicating clearly the conduction of various thyristors during one cycle. 7

http://www.rgpvonline.com

http://www.rgpvonline.com

4. a) Explain with the waveforms the operations of three phase bridge inverter when each is conducting for 120degree, and the resistive load is star connected. 7  
b) What is the purpose of connecting diodes in anti-parallel with thyristors in inverters circuits? 7
5. a) Describe the principle of dc chopper operation. Derive the expression for its average dc output voltage. 7  
b) Describe current commutated chopper with circuit diagram and current and voltage waveforms. 7
6. a) Explain the principle of cycloconverter. 7  
b) How are the frequency and voltage both controlled simultaneously in cycloconverter circuit? 7
7. a) Write the working of single phase A.C. controller when it is supplying an inductive load and plot the waveforms of the output voltage and current if the delay angle is 7  
i) 30degree  
ii) 90degree  
b) A single phase voltage controller with an R-L load is connected to a 110 volts source if  $R=10\text{ Ohms}$  and  $L=20\text{mH}$  and  $\alpha=90\text{degree}$ . Find 7  
i) The Rms output current  
ii) The power delivered to the load  
iii) The power factor
8. Write short notes on any two. 2x7=14  
a) Dual converter  
b) Harmonics and their reduction techniques.  
c) Switch mode power supply  
d) Snubber circuit.

\*\*\*\*\*

http://www.rgpvonline.com

http://www.rgpvonline.com

http://www.rgpvonline.com

http://www.rgpvonline.com