Roll No

MEPS-201

M.E./M.Tech., II Semester

Examination, November 2019

Reactive Power Control and FACTs

Time: Three Hours

Maximum Marks: 70

Note: i) Attempt any five questions.

ii) All questions carry equal marks.

- a) What do you mean by "FACTs Controllers"? What are the advantages and disadvantages of FACTs controllers? Explain in brief.
 - b) State and explain "VSI-based FACTs controllers".
- a) Discuss the equivalent circuit diagram of SVC and its working principle.
 - b) State and explain the following:
 - i) Series-connected FACTs controllers
 - ii) Shunt-connected FACTs controllers
- 3. a) Differentiate between STATCOM and SVC.
 - State and explain the working principle of D-STATCOM with relevant expressions and circuit diagrams.
- 4. a) Explain the following:
 - i) IEEE FACTs controllers
 - ii) SMES FACTs controllers
 - iii) BESS FACTs controllers
 - iv) HPFC FACTs controllers

РТО

http://www.rgpvonline.com

http://www.rgpvonline.com

1-1

- b) Discuss the constructional details and working principles of TC-PAR. What are the advantages of TC-PAR over TCSC?
- 5. a) State and explain the equivalent circuit diagram and working principle of UPFC. What are the merits and demerits of UPFC?
 - b) Differentiate between UPFC and UPQC.
- 6. a) How to enhanced the following system performances by FACTs controllers in multi-machines power systems?
 - i) Power System Oscillations
 - ii) Loadability of the system
 - b) Discuss the following:
 - i) Series-compensation by TCSC
 - ii) Shunt-compensation by SVC
 - iii) Phase angle compensation by TC-PAR.
- 7. a) What do you mean by "TRANSIENT STABILITY"? How to it is minimized by FACTs controllers?

http://www.rgpvonline.com

- b) Define the following:
 - i) SSSC FACTs controllers
 - ii) IPFC-FACTs controllers

Also mention their limitations and significances.

- 8. a) Write a short note on mitigation of SSR by using FACT: controllers.
 - Discuss the constructional features and working principle of GUPFC and GIPFC. Differentiate between GUPF and GIPFC.

MEPS-201